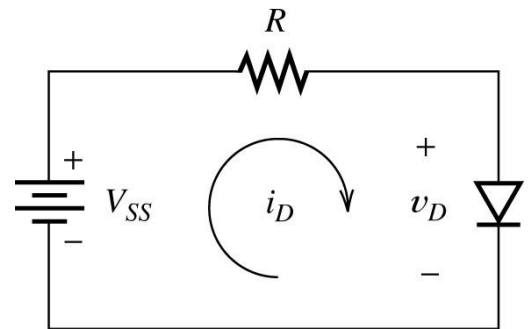


LAST NAME


FIRST NAME

**Problem 1**

- A) Given  $R=200\ \Omega$  &  $V_{SS}=4.0\text{ V}$  Draw the DC load line.  
 B) Use graphical method to obtain the Q point and write down the approximate values for  $I_Q$  and  $V_Q$ .  
 C) Use graphical method to obtain the value of  $r_d$  at the Q point.  
 D) Repeat A), B), and C) for  $V_{SS}=1\text{ V}$ .

**ANSWERS (draw tangents as accurately as possible)**

| $V_{SS}\text{ (V)}$ | $V_{DQ}\text{ (V)}$ | $I_{DQ}\text{ (mA)}$ | $r_{dQ}\text{ (}\Omega\text{)}$ |
|---------------------|---------------------|----------------------|---------------------------------|
| 4.0                 | 1.18                | 14.0                 | 12.1                            |
| 1.0                 | 0.7                 | 1.5                  | 68                              |

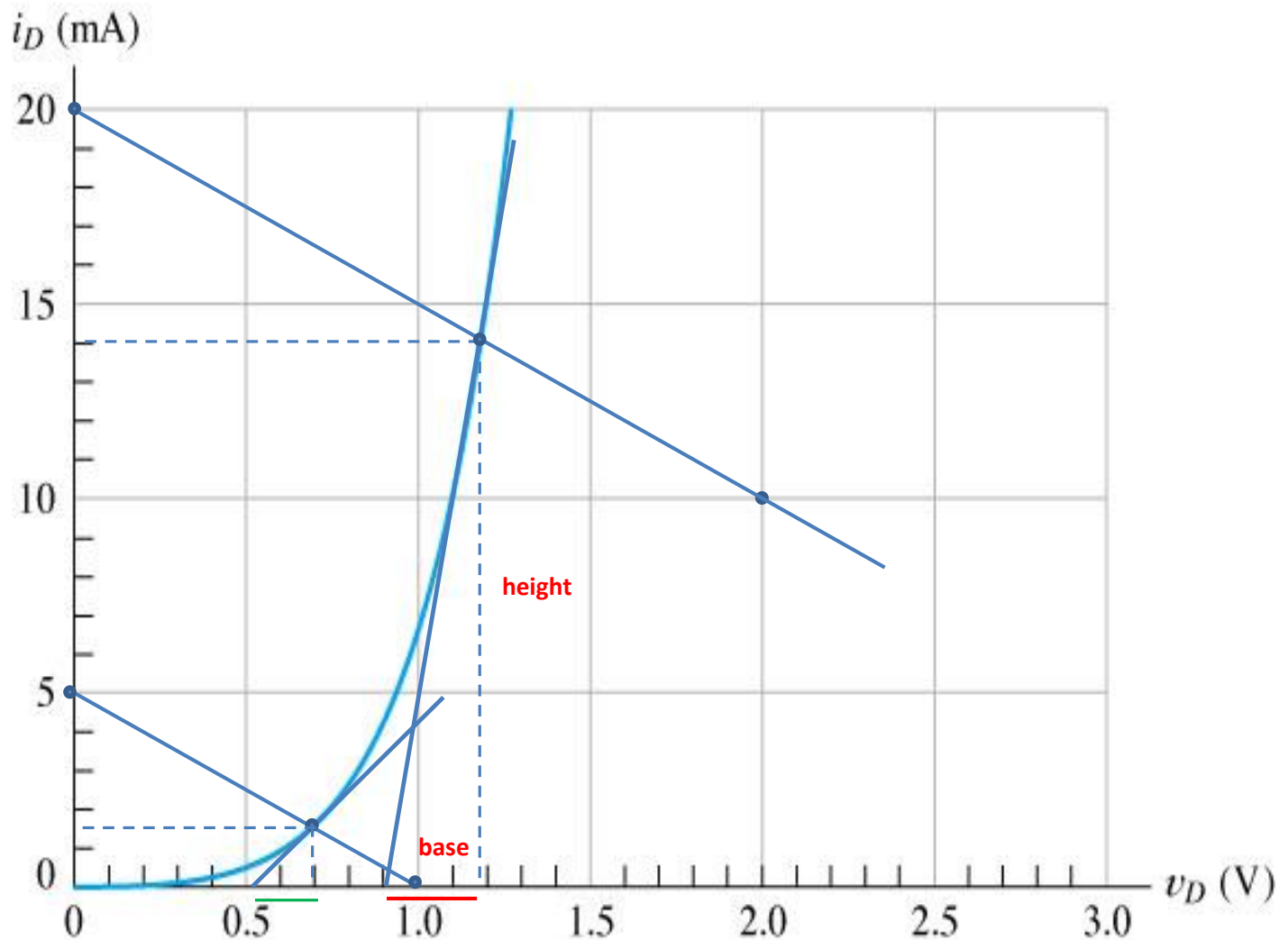

LAST NAME

FIRST NAME

**Problem 1 continued**

**Unit convention :**  $[R] = k\Omega$        $[i] = mA$        $[v] = V$

**Load Lines :**

$KVL \Rightarrow v_D = V_{SS} - Ri_D$  This represents a straight line in the  $v_D - i_D$  space (*load line*)

**Drawing Load Lines :**

Find two points on the line by choosing two values of  $i_D$  and the corresponding  $v_D$  values.

*Case 1:*  $V_{SS} = 4V$  :  $v_D = 4 - 0.2i_D$ .

For example  $A_1$ : choose  $i_D = 20 \Rightarrow v_D = 0$      $B_1$ : choose  $i_D = 10 \Rightarrow v_D = 2$

*Case 2:*  $V_{SS} = 1.0V$  :  $v_D = 1.0 - 0.2i_D$ .

For example  $A_2$ : choose  $i_D = 0 \Rightarrow v_D = 1.0$      $B_2$ : choose  $v_D = 0 \Rightarrow i_D = 5$

**Q - point :** Interception of load line with Diode IV curve

**Dynamic Resistance :**  $r_{dQ} = \frac{1}{\text{slope of tangent}} = \frac{\text{triangle base}}{\text{triangle height}}$


*Case 1:*  $r_{dQ} = \frac{0.17 V}{14 mA} = 12.1 \Omega$       *Case 2:*  $r_{dQ} = \frac{0.17 V}{2.5 mA} = 68 \Omega$

LAST NAME

FIRST NAME

**Problem 2**

Op Amp input resistance is  $\infty$ , output resistance is 0, and open loop gain is  $\infty$  and the power supplies are at +10 and -10 V.  $R_1=2\text{ k}\Omega$ ,  $R_2=1\text{ k}\Omega$ , and  $R_L=4\text{ k}\Omega$ .  $v_{in}=2\text{ V}$ . Find  $v_o$  and current supplied by the Op Amp.

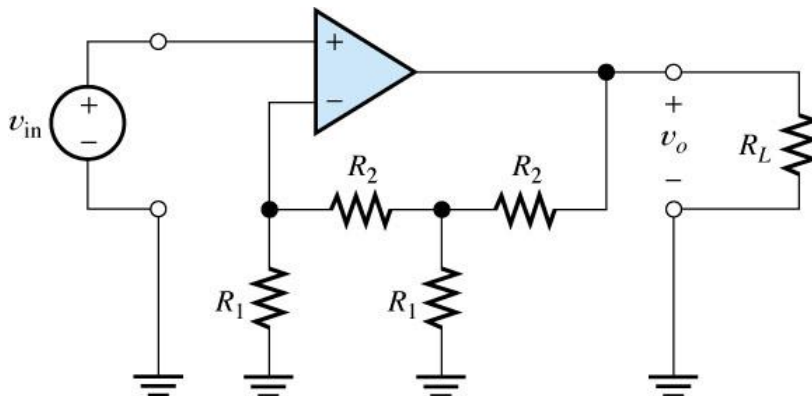**Solution:**

Assume Op Amp is operating in Linear Region *then*  $v_N = v_P$

$$\therefore v_N = 2\text{ V}$$

Node Voltage Equations

$$\begin{cases} \frac{v_N}{R_1} + \frac{v_N - v_A}{R_2} = 0 & \Rightarrow \frac{2}{2} + \frac{2 - v_A}{1} = 0 \Rightarrow 2 + 4 - 2v_A = 0 \Rightarrow v_A = 3\text{ V} \\ \frac{v_A}{R_1} + \frac{v_A - v_N}{R_2} + \frac{v_A - v_o}{R_2} = 0 & \Rightarrow \frac{3}{2} + \frac{3 - 2}{1} + \frac{3 - v_o}{1} = 0 \Rightarrow 3 + 2 + 6 - 2v_o = 0 \Rightarrow v_o = 5.5\text{ V} \end{cases}$$

Note that  $-10 < 5.5 < +10 \Rightarrow -10 < v_o < +10 \Rightarrow$  **Original Assumption IS valid.**

$$I_{Op\ Amp} = \frac{v_o - v_A}{R_2} + \frac{v_o}{R_L} \Rightarrow I_{Op\ Amp} = \frac{5.5 - 3}{2} + \frac{5.5}{4} = 2.625\text{ A}$$